

ECEN405 Lab 1

Keshav Raj 300418412
Lab Partner: Tim Loretto

I. DELIVERABLES

A. 1)

$$30k = \frac{10k}{32.8k(1k)C_1}$$

$$30k = \frac{10k}{32.8M C_1}$$

$$\frac{1}{C_1} = \frac{30k \cdot 32.8M}{10k}$$

$$C_1 = \frac{10k}{30k \cdot 32.8M}$$

$$C_1 = 10.1626nF$$

$$C_1 \approx 10nF$$

B. 2)

In order to find the minimum frequency, R_3 needs to be minimized and R_4 needs to be maximized. By entering the formula into desmos and assigning R_3 to be the X axis and R_4 an adjustable slider, the entire range of frequencies can be investigated.

Fig. 1. Minimum frequency at $R_3 = 0\Omega$ and $R_4 = 100k\Omega$


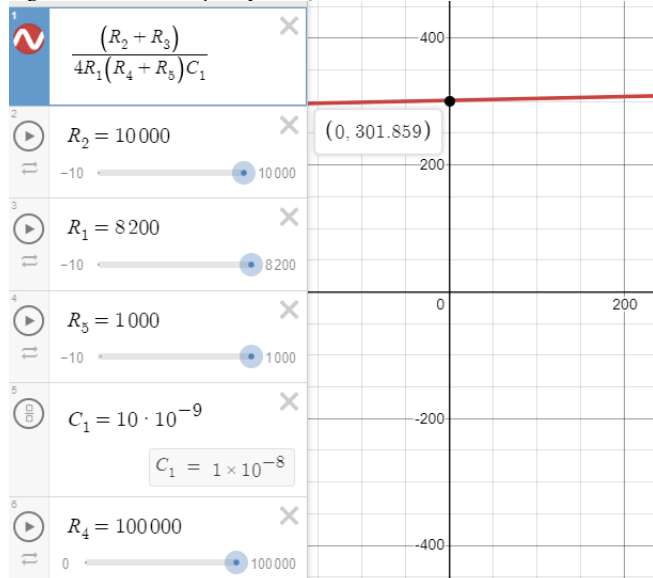


Fig. 2. Maximum frequency when $R_3 = 1M\Omega$ and $R_4 = 0\Omega$

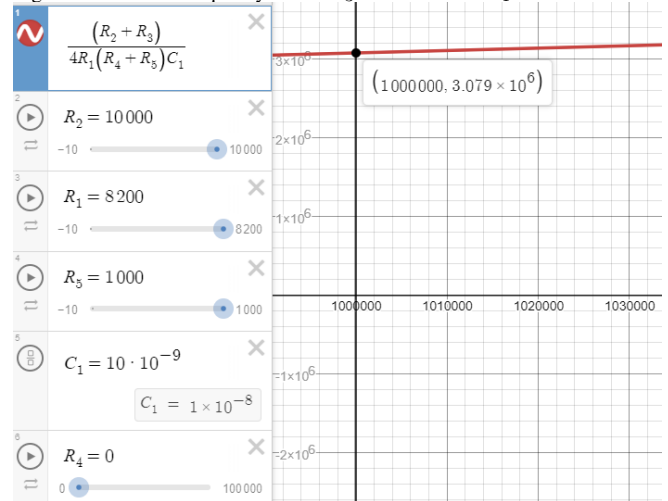

These two figures show that the minimum frequency is 301Hz while the max is 3MHz.

C. 3)

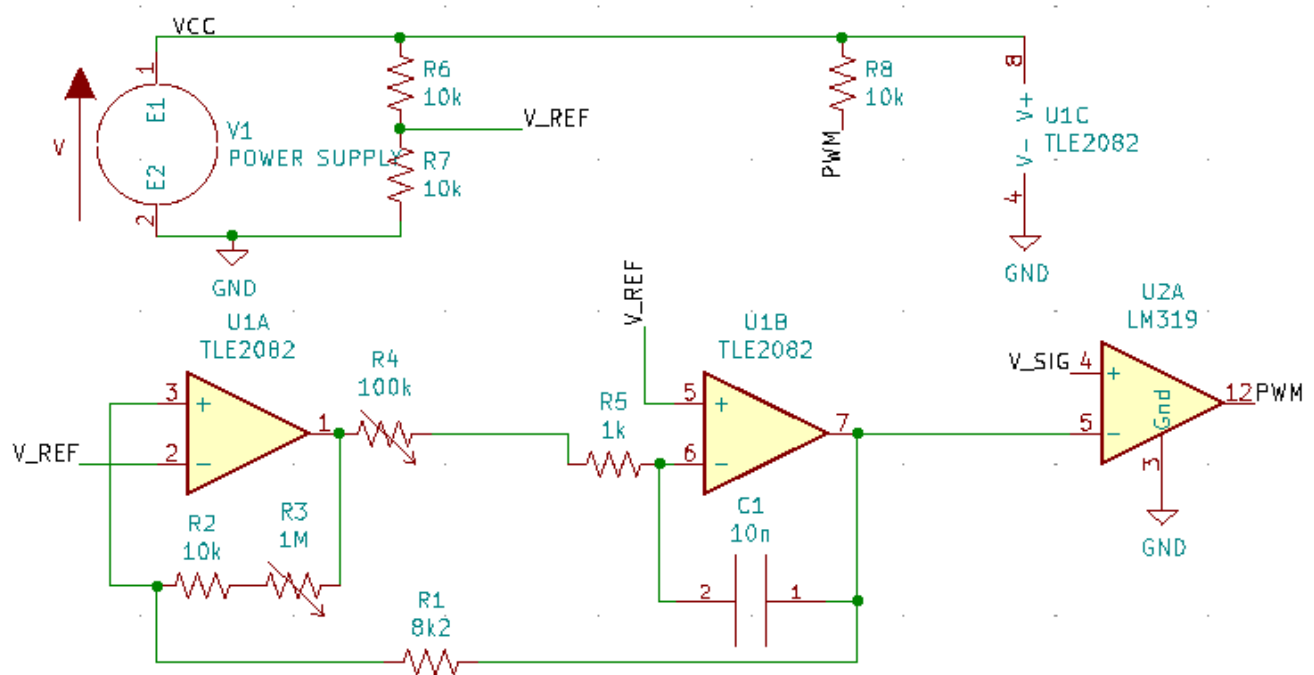


Fig. 3. Schematic of PWM Generator